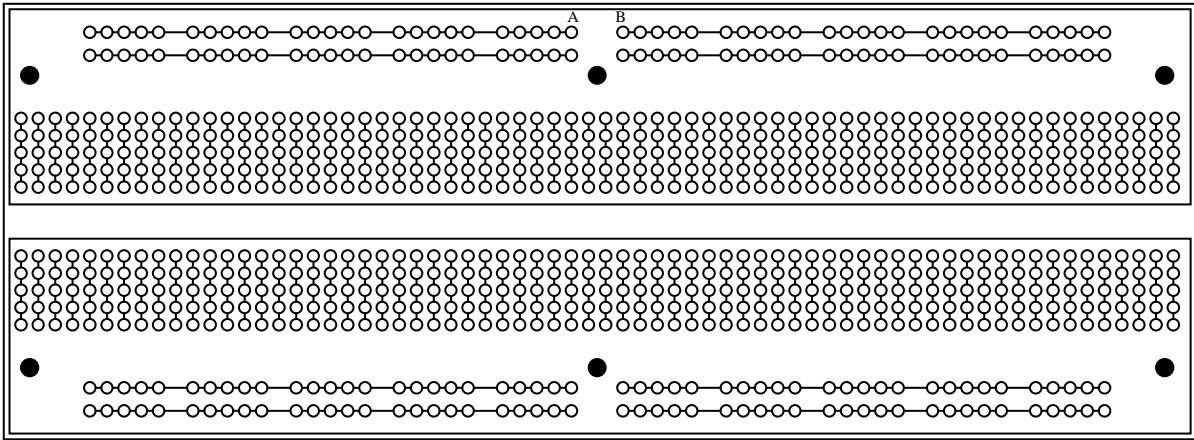




SK-10 Solderless Breadboard (or equivalent)





Internal Connections on the SK-10 Solderless Breadboard

- Notes:
- 1) Lines indicate which holes are connected under the breadboard.
 - 2) To connect two or more wires together, plug them in the same row of holes.
 - 3) Holes A and B are connected on some breadboards (as well as the similar holes on the other horizontal rows).

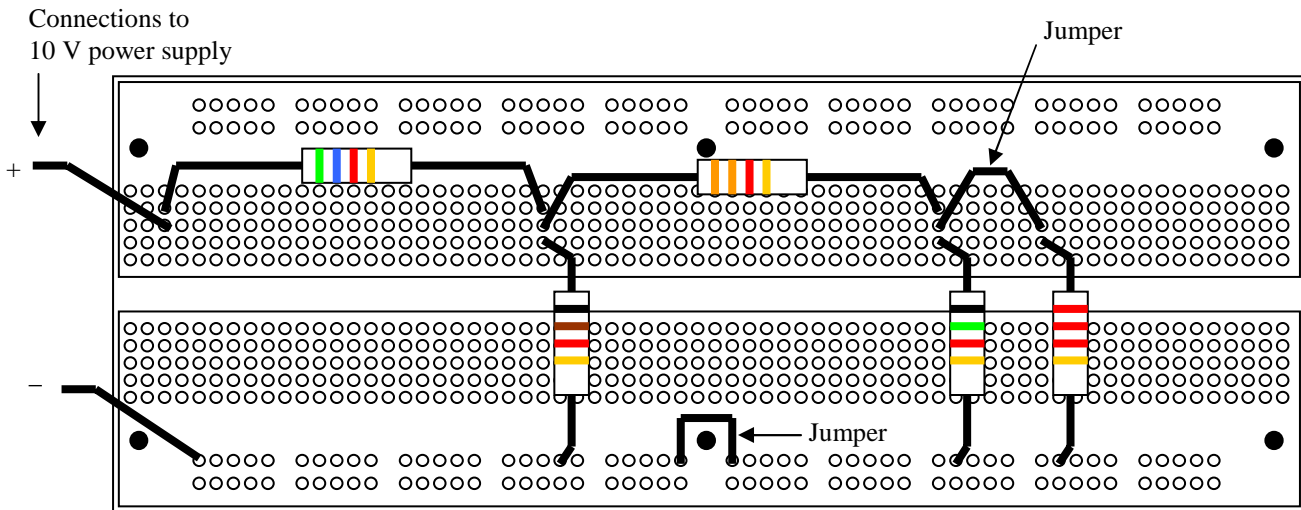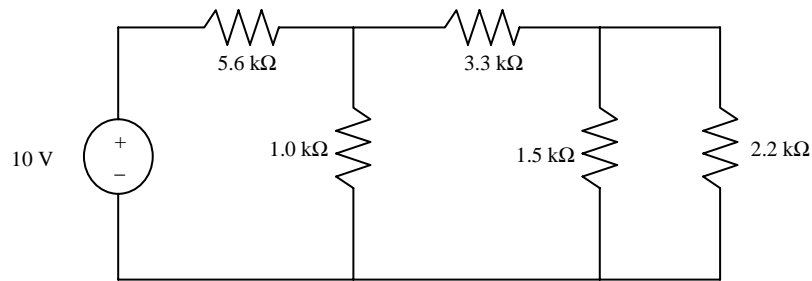Example: Connect the following circuit using the SK-10 solderless breadboard.



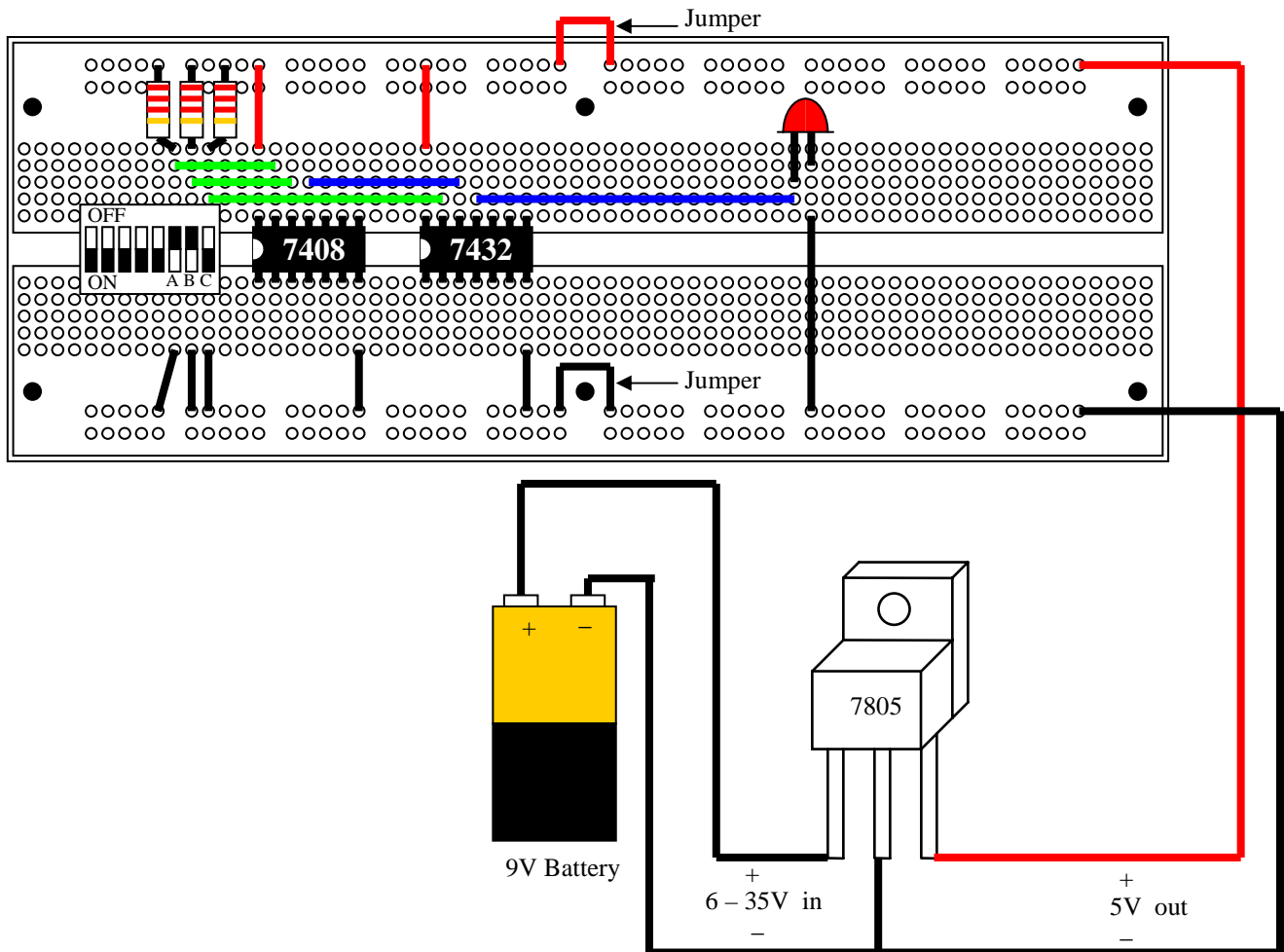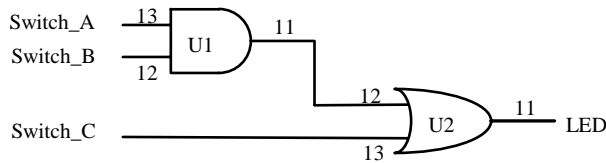Example: Connect the following circuit using the SK-10 solderless breadboard.



Notes:

- 1) The DIP switch operates as follows:
 - ON – Provides a logical 0 (LOW). Closed switch makes connection to ground.
 - OFF – Provides a logical 1 (HIGH). Open switch provides 5V through the 2.2k resistor. (It is often useful to install the switch *upside down* so that ON (LOW) is on the bottom.)
- 2) The switch positions shown above (darkened) provide an input of 110 causing the red LED to light indicating that the output is logical 1 (HIGH).
- 3) Cutting wires to length and using a wire color scheme makes for a neat circuit that is easy to troubleshoot. In the circuit above the following color scheme was used:
 - RED – 5V
 - BLACK – Ground (0V)
 - GREEN – Switch connections
 - BLUE – Other connections