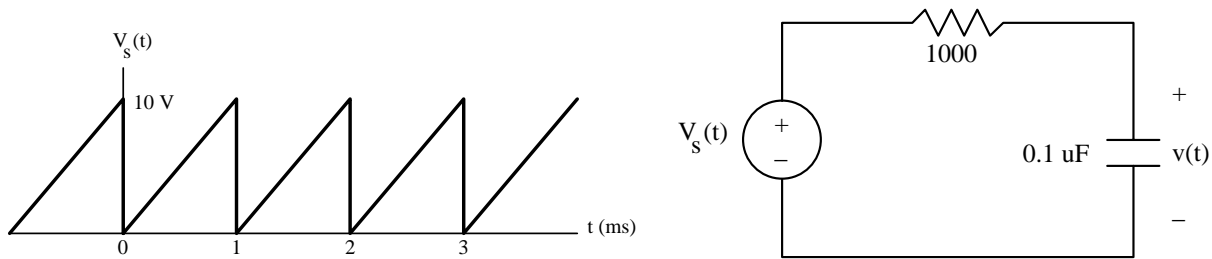


## Analysis of a Series RC Circuit with a Ramp Wave Input


**Problem:** Determine the RMS value of the capacitor voltage,  $v(t)$ , in the circuit shown below. The input voltage,  $V_s(t)$ , is an infinite periodic 0 to 10V ramp waveform.



**Solution:**  $V_s(t)$  should first be represented by a Fourier series. The Fourier series shown below was determined in a previous problem.


$$V_s(t) = 5 - \frac{10}{\pi} \sin(2000\pi t) - \frac{10}{2\pi} \sin(4000\pi t) - \frac{10}{3\pi} \sin(6000\pi t) - \frac{10}{4\pi} \sin(8000\pi t) - \dots$$

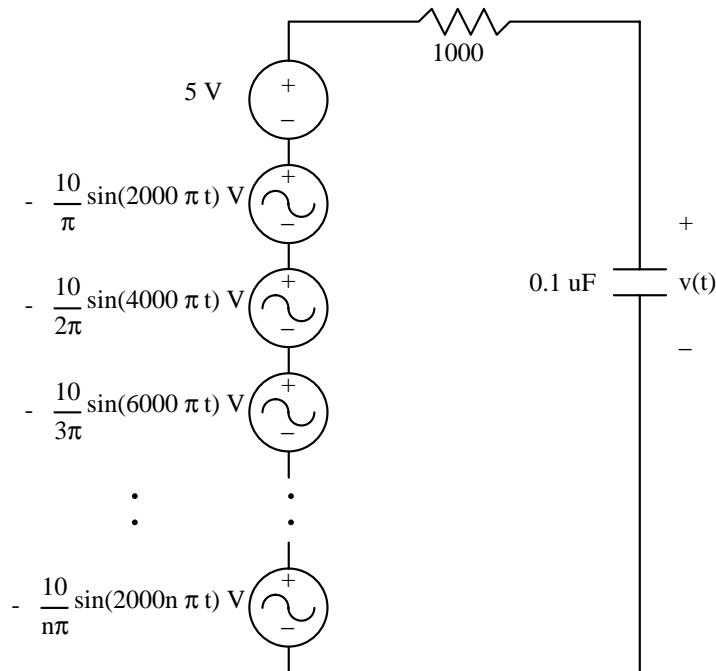We can now replace the ramp voltage source by an infinite number of sinusoidal voltage sources as shown below:




Now using superposition the circuit can be analyzed once for each source with all other sources killed (shorted). Note that the capacitor impedance changes for each circuit.

**DC source only:**

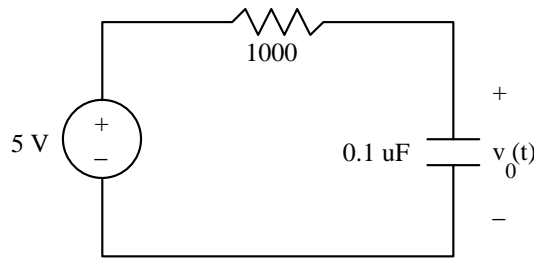


Equivalent Circuit:

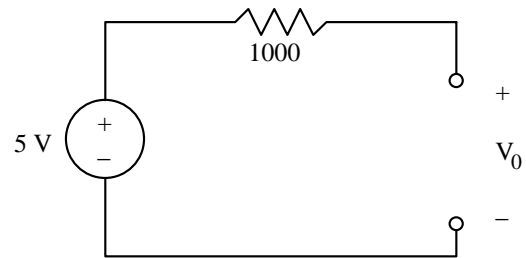


$$\boxed{V_0 = 5 \text{ V}} \text{ (DC component)}$$

**First harmonic source only:**

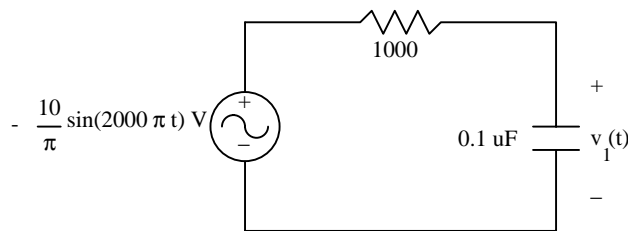

AC Equivalent Circuit:

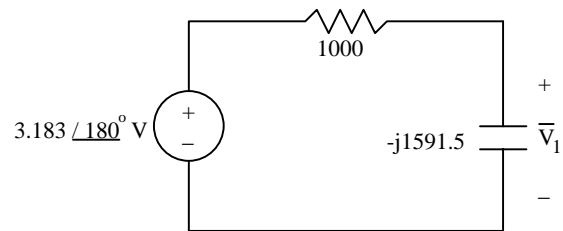


$$\bar{V}_1 = 3.183 \angle 180^\circ \cdot \left[ \frac{-j1591.5}{1000 - j1591.5} \right]$$


$$\bar{V}_1 = 2.695 \angle 147.9^\circ$$

$$\boxed{V_1 = 2.695 \text{ V}} \text{ (1}^{\text{st}} \text{ harmonic component)}$$

**Second harmonic source only:**

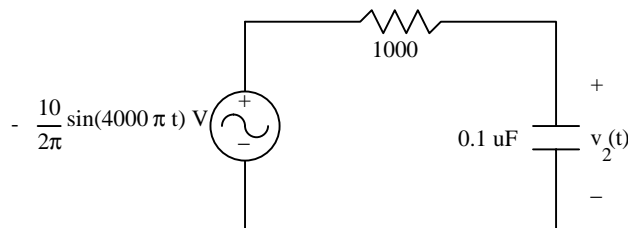


AC Equivalent Circuit:

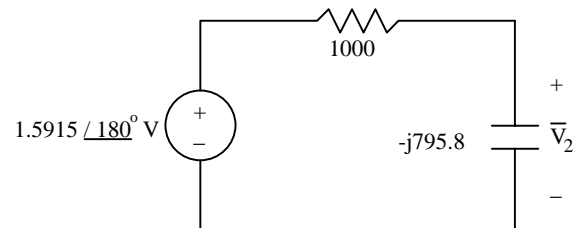


$$\bar{V}_2 = 1.5915 \angle 180^\circ \cdot \left[ \frac{-j795.8}{1000 - j795.8} \right]$$

$$\bar{V}_2 = 0.991 \angle 128.5^\circ$$

$$\boxed{V_2 = 0.991 \text{ V}} \text{ (2}^{\text{nd}} \text{ harmonic component)}$$

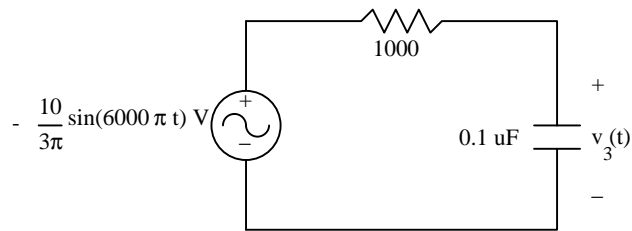**Third harmonic source only:**


AC Equivalent Circuit:

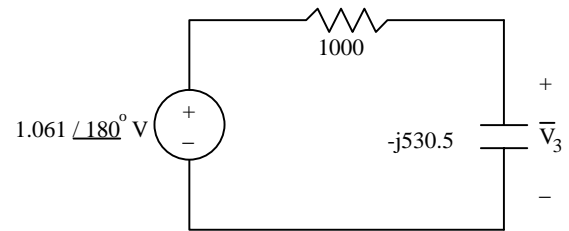


$$\bar{V}_3 = 1.061 \angle 180^\circ \cdot \left[ \frac{-j530.5}{1000 - j530.5} \right]$$

$$\bar{V}_3 = 0.4972 \angle 117.9^\circ$$

$$\boxed{\bar{V}_3 = 0.4972 \text{ V}} \text{ (3}^{\text{rd}} \text{ harmonic component)}$$

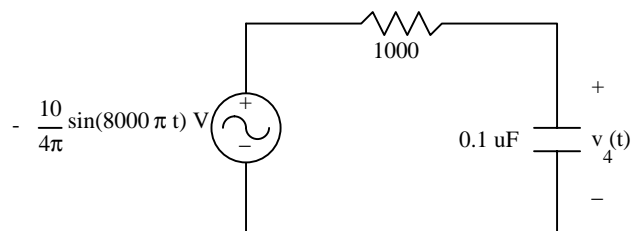**Fourth harmonic source only:**



AC Equivalent Circuit:

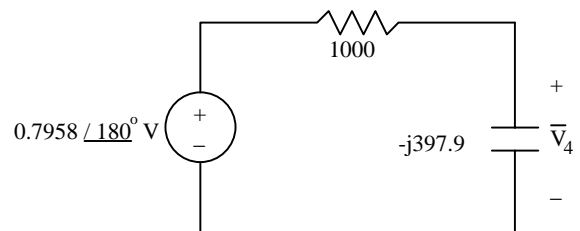

$$\bar{V}_4 = 0.7958 \angle 180^\circ \cdot \left[ \frac{-j397.9}{1000 - j397.9} \right]$$

$$\bar{V}_4 = 0.2942 \angle 111.6^\circ$$

$$\boxed{\bar{V}_4 = 0.294 \text{ V}} \text{ (4}^{\text{th}} \text{ harmonic component)}$$

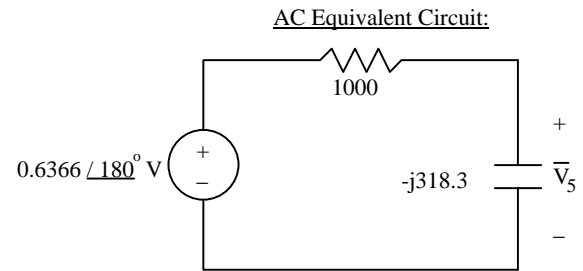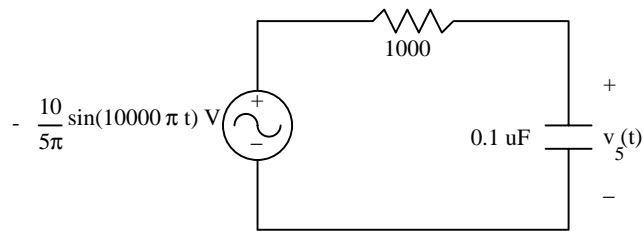**Fifth harmonic source only:**

$$\bar{V}_5 = 0.6366 \angle 180^\circ \cdot \left[ \frac{-j318.3}{1000 - j318.3} \right]$$

$$\bar{V}_5 = 0.1931 \angle 107.6^\circ$$

$$\boxed{V_5 = 0.193 \text{ V}} \text{ (5}^{\text{th}} \text{ harmonic component)}$$

**Total capacitor voltage:**

In general,  $V_{\text{RMS}} = \sqrt{V_0^2 + \frac{V_1^2 + V_2^2 + V_3^2 + V_4^2 + \dots}{2}}$  (using **peak** sinusoidal values)

In the example above,  $V_{\text{RMS}}$  can be approximated by using the DC component and the first 5 harmonics as follows:

$$V_{\text{RMS}} \approx \sqrt{5^2 + \frac{2.695^2 + 0.991^2 + 0.4972^2 + 0.2942^2 + 0.1931^2}{2}}$$

$$\boxed{V_{\text{RMS}} \approx 5.414 \text{ V}}$$

On the following page MATHCAD is used to determine  $V_{\text{RMS}}$  by including 100 harmonics.