


Homework Assignment #3 – Analyzing Circuits with Laplace Transforms

Reading Assignment:


Ch. 13, Sect. 1-5, 7 in *Electric Circuits, 9th Edition* by Nilsson
Ch. 4, Sect. 4 in *Linear Signals & Systems, 2nd Ed.* by Lathi
Handout: Laplace Transform Properties and Common Laplace Transform Pairs
Lecture notes

Problem Assignment:

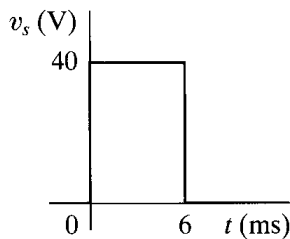- 1) Work the following problems from Ch. 13 of *Electric Circuits, 9th Edition* by Nilsson: 9, 10, 11, 29(a & c only), 46, 50, 57a, 70a (find $H(s)$ then the impulse response, $h(t)$)
- 2) The voltage waveform in Figure (a) below is applied to the input of the circuit shown in Figure (b) below. The initial voltage on the capacitor is zero.
 - A) Write an expression for $v_s(t)$ using unit step functions
 - B) Use Laplace transforms to solve for $v_o(t)$
 - C) Sketch $v_o(t)$ versus t .




(a)

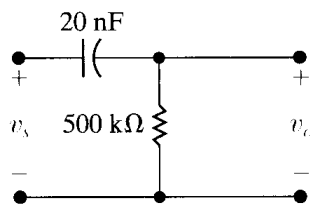

(b)

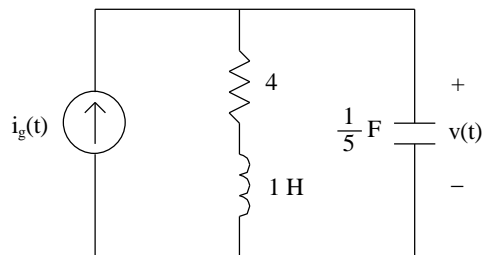- 3) Work problem 4.4-7 in *Linear Signals & Systems, 2nd Ed.* by Lathi:
- 4)
 - A) Determine the transfer function $H(s) = V(s)/I_g(s)$ for the circuit shown below.
 - B) Determine the impulse response [i.e., find $v(t)$ if $i_g(t) = \delta(t)$ A].
 - C) Determine the unit step response [i.e., find $v(t)$ if $i_g(t) = u(t)$ A].



MATLAB Problems (Extra Credit):

Put all problems in a single MATLAB program with an initial block of comments (name, course assignment number, etc) and add a comment identifying each part. Include a printout of the program and the output. Check your results to make sure that they are correct.

- 1) Solve problem 13-9 using MATLAB. In particular, enter the s-domain equation(s) used to analyze the circuit and solve the equation(s) using *solve* (. Use *ilaplace* () to find the corresponding time domain expressions.
- 2) Repeat for problem 13-10.

Selected Answers:

13.10) $v_o(t) = 137.5 + 80.04e^{-5,000t} \cos(5,000t + 141.34^\circ)u(t)$ V

or $v_o(t) = 137.5 - e^{-5,000t} [62.5\cos(5,000t) + 50\sin(5000t)]u(t)$ V

13.11) a) $i_L(0) = 5A$, $v_C(0^-) = -70V$ b) $V_o(s) = -70(s + 20/7)/(s^2 + 10s + 50)$

c) $v_o(t) = 76.2e^{-5t} \cos(5t - 156.8^\circ)u(t)$ V

or $v_o(t) = e^{-5t} [-70\cos(5t) - 30\sin(5t)]u(t)$ V

13.46) $v_o(t) = 40e^{-5,000t} \cos(10,000t + 90^\circ)u(t)$ mV = $-40e^{-5,000t} \sin(20,000t)u(t)$ mV

13.57a) $H(s) = \frac{I_o(s)}{I_g(s)} = \frac{s^2}{s^2 + 2000s + 5 \times 10^7}$

13.70) a) $H(s) = \frac{0.8}{s+1}$, $h(t) = 0.8e^{-t}u(t)$

2) $v_o(t) = 40e^{-100t}u(t) - 40e^{-100(t-0.006)}u(t-0.006)$ V

4.4-7) $y(t) = e^{-2t} [1.5\cos(3t) - 5/6\sin(3t)]u(t)$ V = $1.716e^{-2t} \cos(3t + 29.1^\circ)u(t)$ V

3) a) $H(s) = \frac{V(s)}{I_g(s)} = \frac{5s + 20}{s^2 + 4s + 5}$

b) $v(t) = h(t) = e^{-2t} [5\cos t + 10\sin t]u(t)$ V

c) $v(t) = 4 - e^{-2t} [4\cos t + 3\sin t]u(t)$ V