


Homework Assignment #10

Reading Assignment:

Chapter 6, Sections 1-6, in Logic and Computer Design Fundamentals, 4th Edition, by Mano.

Problem Assignment:

1. Use a timing diagram to determine the counting sequence for the counter shown in Figure 1 (next page) if the counter begins with count 0. As a minimum, include waveforms for the input clock, SA, RA, SB, RB, SC, RC, Q_A, Q_B, and Q_C. Q_A is the MSB.
2. Chapter 6 problems 5, 6, 8, 11, 14
3.
 - A) Sketch the waveforms CP, A, B, C, D, Q1, and Q2 for the circuit shown in Figure 2 (next page).
 - B) For how many clock pulses is Q1 HIGH? For how many clock pulses is Q2 HIGH?
 - C) Modify the circuit so that Q1 goes HIGH at the end of count 7 and stays HIGH for 2 clock pulses. Q2 should go HIGH at the end of count 9 and remain HIGH for 11 clock pulses.
4. Design a circuit to produce the following waveforms:

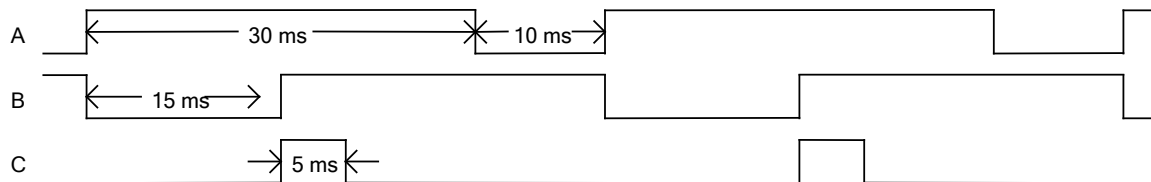

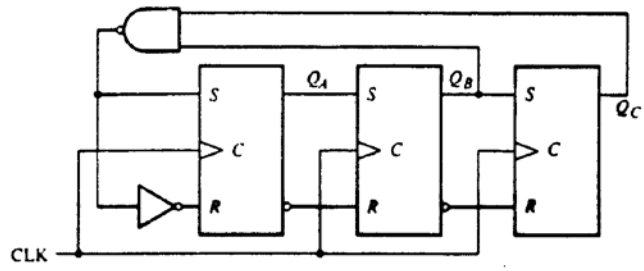


Figure 1

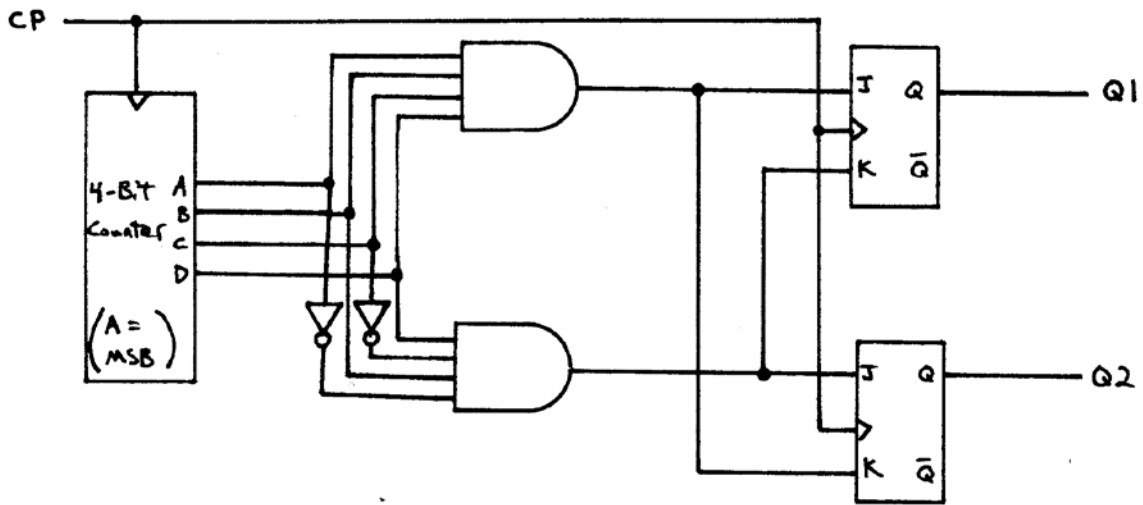


Figure 2