

Homework Assignment #4

Reading Assignment:

Chapter 3 in the textbook Logic and Computer Design Fundamentals, 5th Edition by Mano

Problem Assignment:

- 1) Chapter 3 problems: 1, 2, 3, 4, 6, 8, 9, 10, 20
Hint for 3-3: It is best to list the inputs in normal counting order to make it easy to fill out Kmaps.
Hint for 3-6: The light should turn on when an odd number of switches are in the ON position.
- 2) Design a driver circuit for a common-anode 7-segment display that operates as follows:
 - The display should show 0-5 for the corresponding BCD inputs
 - The display should be blank for inputs 6 – 15
 - Recall that a LOW output is required to light a segment on a common-anode display
 - Show the truth table, the Kmaps used to determine the 7 output expressions (minimal SOP), and the logic diagram.
- 3) See page 2.

Selected Answers:

- 3-1) $F = XZ + XY + YZ$
3-3) $B3 = G3$, $B2 = G3 \oplus G2 + G3G1$, etc.
3-4) a) $W = X1X2X3 + X4X5X6 + \dots$
b) $W = X5(X1X9 + X2X8 + \dots) + \dots$
3-6) $Z = X1 \oplus X2 \oplus X3$ (if odd parity is used)
3-8) $S0 = C$, $S1 = 0$, $S2 = A'BC' + ABC'$, $S3 = A'BC + AB'C$, etc
3-9) $S0 = B'C'D + B'CD' + AB' + AC'D' + A'BCD$, etc
3-20) Algebraically show that $F = XY + X'Y'$
2) $a = A + BC + BD' + B'C'D$
 $b = A + BC + BD$
 $c = A + BC + CD'$
etc

(continued)

Name: _____

EGR 270 HW #4 (continued) – **Turn in this worksheet as part of the assignment**

3) Given the following input waveforms ABCD for problem 3-10, sketch the outputs WXYZ using the grid provided below. This sheet can be printed out, filled in, and turned in with the assignment.

