

Homework Assignment #6

Reading Assignment:

Chapter 3 and Section 5-2 in the textbook Logic and Computer Design Fundamentals, 5th Edition by Mano

Problem Assignment:

- 1) (72 pts or 9 pts each) Chapter 3 problems: 50, 51, 52, 53, 54, 55, 57, 64
- 2) (10 pts) Implement a full-adder using a PAL on the worksheet provided.
- 3) (10 pts) Implement a 2x1 multiplexer using a PLA on the worksheet provided..
- 4) (8 pts) Complete the timing diagram for a full adder on the worksheet provided.

Selected Answers:


3-52) a) 01001 b) 10000 (= -10000)

3-53) a) 01001 b) 00000

3-54) Check the results by converting the results back to decimal. Example: $36 + (-24) = 12$

3-55) a) 100000 (-32) b) 110001 (-15) c) 011111 (-33) overflow error

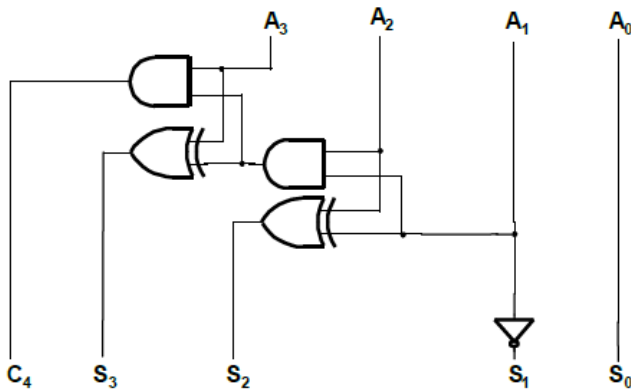3-57) Show the original adder circuit and label all values on the circuit to show how it reduces. The result is shown below:




3-64) (3 of 5 parts shown)

	S	A	B	C ₄	S ₃	S ₂	S ₁	S ₀
a)	0	0111	0111	0	1	1	1	0
b)	1	0100	0111	0	1	1	0	1
c)	1	1101	1010	1	0	0	1	1


EGR 270 HW #6 (continued) – **Turn in this worksheet as part of the assignment**

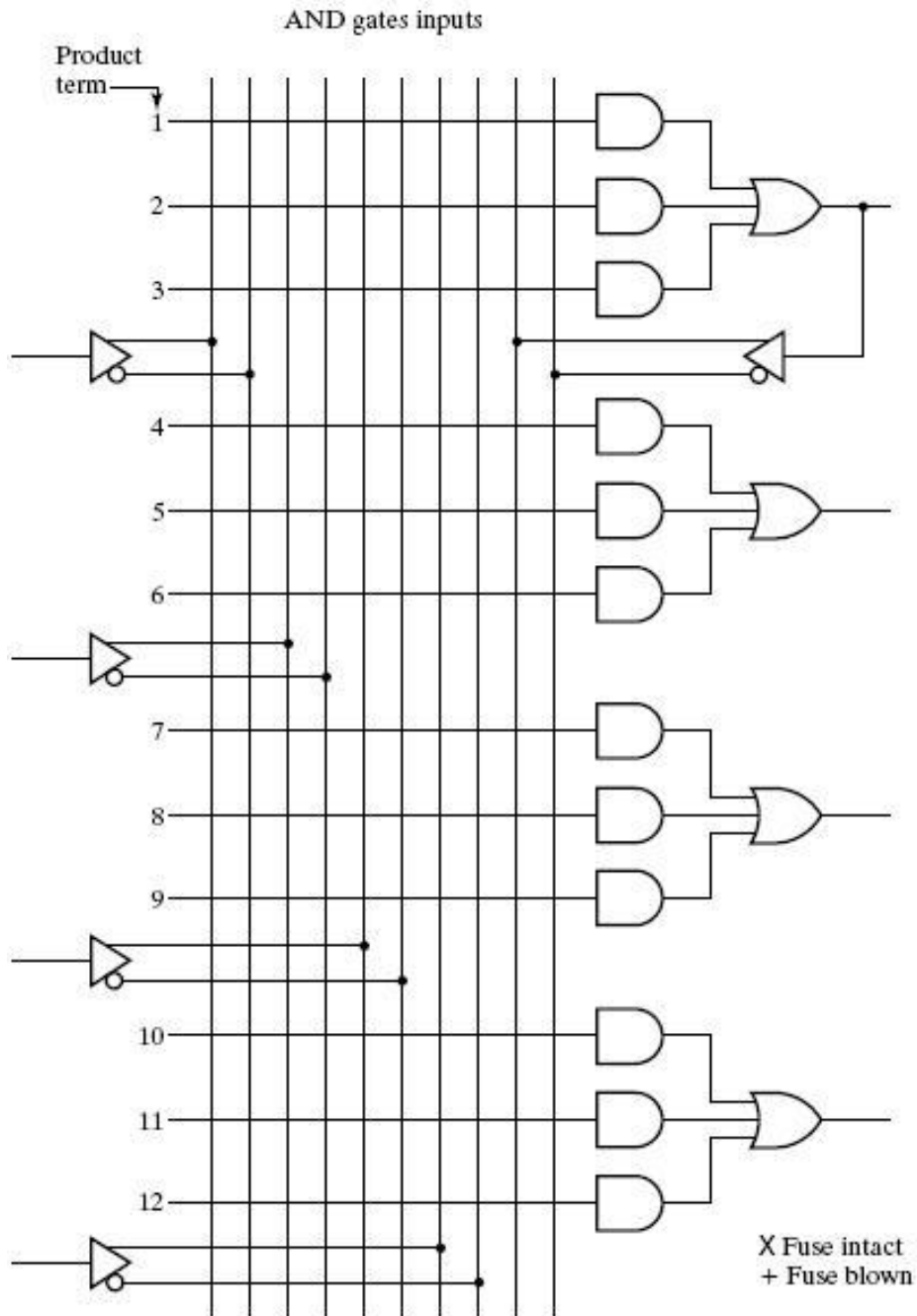- 2) (10 pts) Implement a full-adder using the PAL shown below (similar to the one used in class and to Figure 5-10 in the textbook).
- Show the equations for the outputs of the full adder in SOP form.
 - Label the inputs and the outputs on the diagram below. The inputs should be labeled A, B, and C_i . The outputs should be labeled S and C_o .
 - Add X's to show all the connections required in the PAL.



EGR 270 HW #6 (continued) – **Turn in this worksheet as part of the assignment**

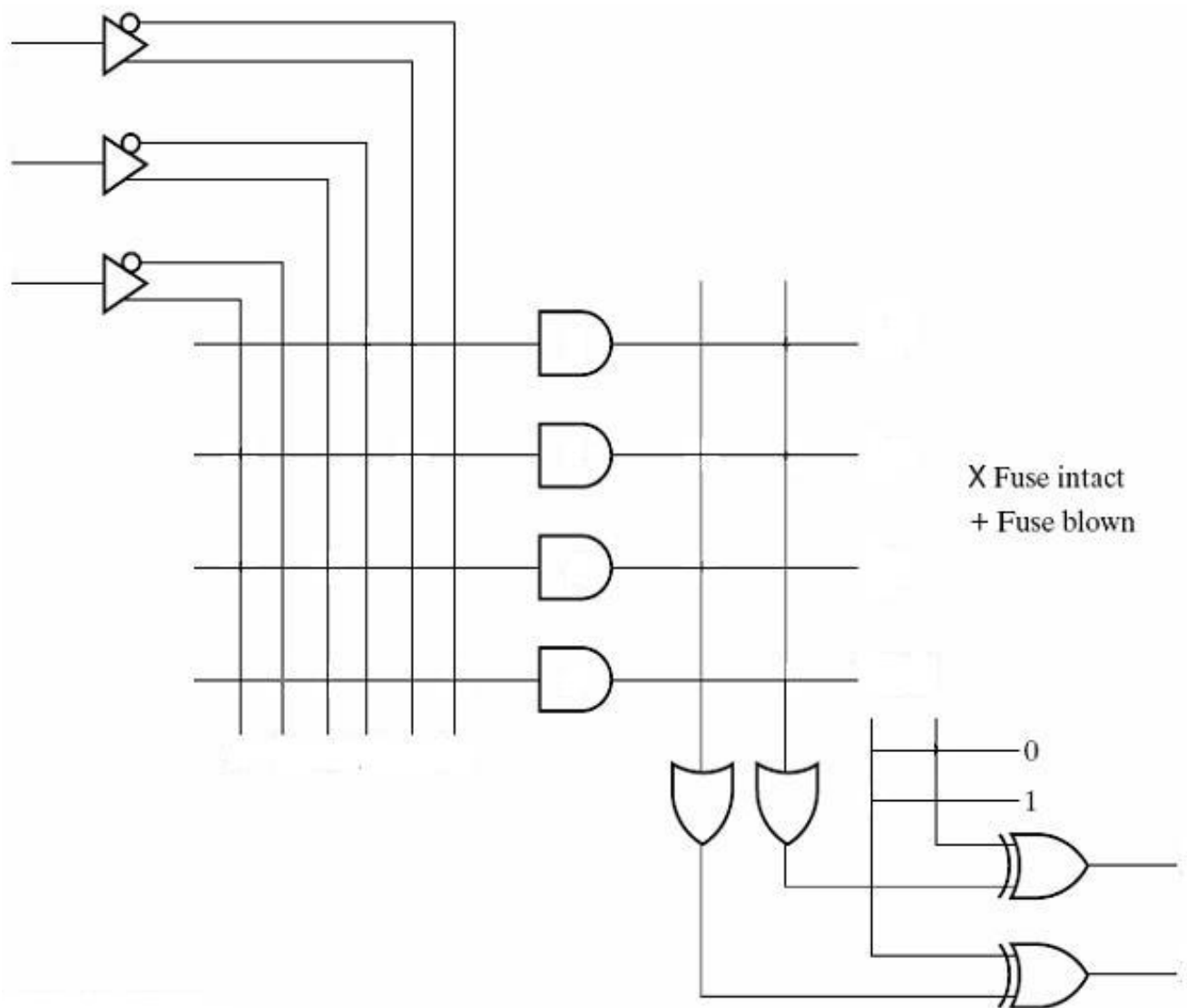- 3) (10 pts) Implement a 2x1 multiplexer using the PLA shown below (similar to the one used in class and to Figure 5-8 in the textbook).
- Show the equation for the output of the multiplexer in SOP form.
 - Label the inputs and the outputs on the diagram below. The inputs should be labeled I0, I1, and S, where S is the select line. The output should be labeled Y
 - Add X's to show all the connections required in the PLA.



Name: _____

EGR 270 HW #6 (continued) – **Turn in this worksheet as part of the assignment**

4) Timing Diagrams: (8 pts) Waveforms Ci, A, and B shown below are the inputs to a full adder. Sketch the outputs Co and S.

