

Homework Assignment #7


Reading Assignment:

Chapter 4 in the textbook Logic and Computer Design Fundamentals, 5th Edition by Mano
Online supplement “Design and Analysis using JK and T Flip-Flops”
(http://wps.pearsoned.com/ecs_mano_lcd_f_5/)

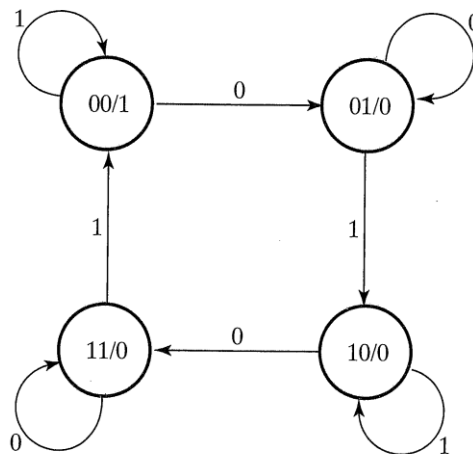Problem Assignment:


- Chapter 4 problems: 4, 5, 7, 8, 10, 11, 13
- Problems 4 and 5 in the online supplement “Design and Analysis using JK and T Flip-Flops.” These problems are also shown below. Note: Problem 4 should refer to the figure shown below, not Figure 6-40, in the text.

- *Design a sequential circuit for the state diagram given in Figure 6-40 of the text (see Reference 1) using JK flip-flops.**
- *Design a sequential circuit with two JK flip-flops A and B and two inputs E and X. If E = 0, the circuit remains in the same state, regardless of the value of X. When E = 1 and X = 1, the circuit goes through the state transitions from 00 to 01 to 10 to 11, back to 00, and then repeats. When E = 1 and X = 0, the circuit goes through the state transitions from 00 to 1 to 10 to 01, back to 00, and then repeats.**



Selected Answers (Partial Solutions):


4-4)

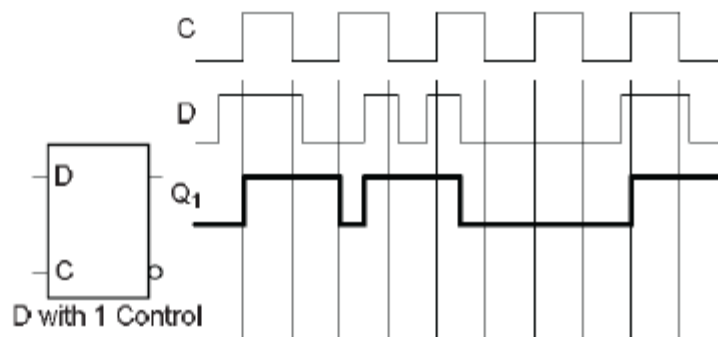

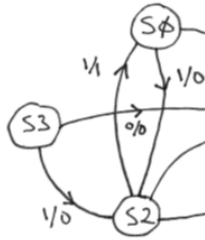4-5)


- S0 - 00
- S1 - 01
- S2 - 10
- S3 - 11

Partial state diagram (Mealy model) shown below:




4-7.*

Present state			Input	Next state		
A	B	C	X	A	B	C
0	0	0	0	1	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	0	0	1
1	0	0	0	1	1	0
1	0	0	1	0	1	0
1	0	1	0	0	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	1

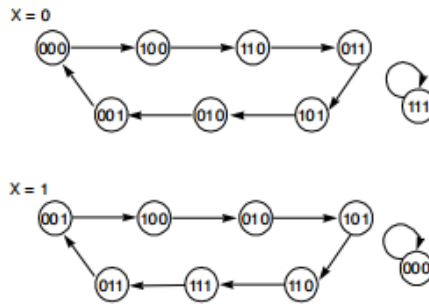

State diagram is the combination of the above two diagrams.

4-8)

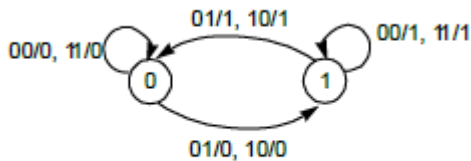

Format: XY/S

4-13.*

Present state		Input	Next state	
A	B	X	A	B
0	0	0	0	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	1

D_A		B	
		1	
A	1	1	1
		X	

$$D_A = A\bar{X} + \bar{B}X$$

D_B		B	
			1
A	1	1	1
		X	

$$D_B = AX + B\bar{X}$$

Logic diagram not given.

Online Supplement Problem 4) $J_A = K_A = XB$, $J_B = X'$, $K_B = X$

Online Supplement Problem 5) $J_A = K_A = EXB + EX'B'$, $J_B = K_B = E$