

PSPICE Assignment #1

PSPICE Analysis of Combinational Logic Circuits

Reference:

Handout: Sample PSPICE Report

PSPICE Example: "*Combinational Logic Circuit*" (File: LOGIC1.OPJ)

PSPICE Example: "*Implementing Functions with a 4 x 16 Decoder*" (File: DECODER.OPJ)

Assignment Description:

Use Cadence Capture version 16.5 or later for this assignment.

1. Custom Combinational Logic Circuit:

A certain function f is defined as follows:

$f(A, B, C, D) = \Sigma(\text{first 5 unique digits of your StudentID} + \text{minterms 12 and 15})$.

Example: If your StudentID is 2286435 then your first 5 unique digits are 2, 8, 6, 4, and 3, so f is defined as follows: $f(A, B, C, D) = \Sigma(2, 3, 4, 6, 8, 12, 15)$. If your StudentID has less than 5 unique digits, add minterm(s) 10 and/or 14.

Let binary waveforms for A, B, C, and D be defined as follows:

A - Clock with a frequency of 5 kHz, initial value is LOW

B - Clock with a frequency of 10 kHz, initial value is LOW

C - Clock with a frequency of 20 kHz, initial value is LOW

D - Clock with a frequency of 40 kHz, initial value is LOW

The 4 waveforms A,B,C,D represent a 4-bit binary code that varies from 0 to 15 in order.

A. SOP Implementation:

- 1) Determine by hand a minimal Sum Of Products (SOP) expression for the function f described above using a Karnaugh map.
- 2) Use PSPICE to implement the SOP expression above using only AND, OR and NOT gates. Use Digital Clocks for A, B, C, and D as described above. Add labels to define all inputs and outputs by standard names. Add text to *all PSPICE schematics*, including name, course, assignment number, problem number, and a brief description.
- 3) Analyze the circuit and create a graph of A, B, C, D, and f above as well as a bus defining the decimal value of the 4 waveforms {A, B, C, D}. The length of the timing diagram should be such that all 16 possible combinations of A, B, C, and D are shown in order. Verify that f is HIGH for each minterm as described above. Include an appropriate title on the graph, such as "**SOP implementation of $f(A,B,C,D) = \text{Sum}(\text{your minterms})$ ".**
- 4) Discuss the results.

B. POS Implementation:

Repeat part 1A above for a Product Of Sums (POS) implementation of f .

C. 8x1 Multiplexer Implementation:

- 1) Use a *multiplexer implementation table* by hand to determine the appropriate connections to be used in order to implement the function f described above. Be aware that A is the MSB and D is the LSB. Add labels to define all inputs and outputs by standard names.
- 2) Use PSPICE to implement the multiplexer circuit above using 74151A 8x1 multiplexer. Use Digital Clocks for A, B, C, and D as described above.
- 3) Analyze the circuit and graph A, B, C, D, and f above as well as a bus defining the decimal value of the 4 waveforms {A, B, C, D}. The length of the timing diagram should be such that all 16 possible combinations of A, B, C, and D are shown in order. Verify that f is HIGH for each minterm as described above. Include an appropriate title on the graph.
- 4) Discuss the results.

D. 4 x 16 Decoder Implementation:

- 1) Implement either the SOP function of part A or the POS function of part B using two 3x8 decoders (using two 74155 IC's) to form a 4 x 16 decoder. Add labels such as D0, D2, etc., to all used decoder outputs
- 2) Analyze the circuit and graph A, B, C, D, f , all used decoder outputs, and a bus defining the decimal value of the 4 waveforms {A, B, C, D}. The length of the timing diagram should be such that all 16 possible combinations of A, B, C, and D are shown in order. Verify that f is HIGH for each minterm as described above. Include an appropriate title on the graph.
- 3) Discuss the results. Do the used decoder outputs (D0, D1, etc) appear as expected? Explain.

E. Comparison of parts 1A, 1B, 1C, and 1D:

Compare the results of parts 1A, 1B, 1C, and 1D. Were they all identical? Which method do you prefer?

2. 4-Bit Magnitude Comparator:

Use PSPICE to implement a 4-bit magnitude comparator circuit using a 7485. Add 4 clocks to the schematic defined as follows:

- A - Clock with a frequency of 5 kHz, initial value is LOW
- B - Clock with a frequency of 10 kHz, initial value is LOW
- C - Clock with a frequency of 20 kHz, initial value is LOW
- D - Clock with a frequency of 40 kHz, initial value is LOW

Connect the waveforms to the inputs indicated below:

- | | |
|--------------------|--------------------|
| A3 - Clock A (MSB) | B3 - Clock D (MSB) |
| A2 - Clock B | B2 - Clock B |
| A1 - Clock C | B1 - Clock A |
| A0 - Clock D | B0 - Clock C |

Note that the magnitude comparator will be comparing the binary value of ABCD with the binary value of DBAC.

Use PROBE to form a timing diagram of A, B, C, D, and the 3 magnitude comparator outputs (in order). Also show two buses, one defining the decimal value of {A, B, C, D} and the other defining the decimal value of {D, B, A, C}. The length of the timing diagram should be such that all 16 possible combinations of A, B, C, and D can be seen in order. Verify that the magnitude comparator yields the correct results in each case. *Clearly discuss the output graph. Explain how the output graph shows that the circuit is performing properly.*