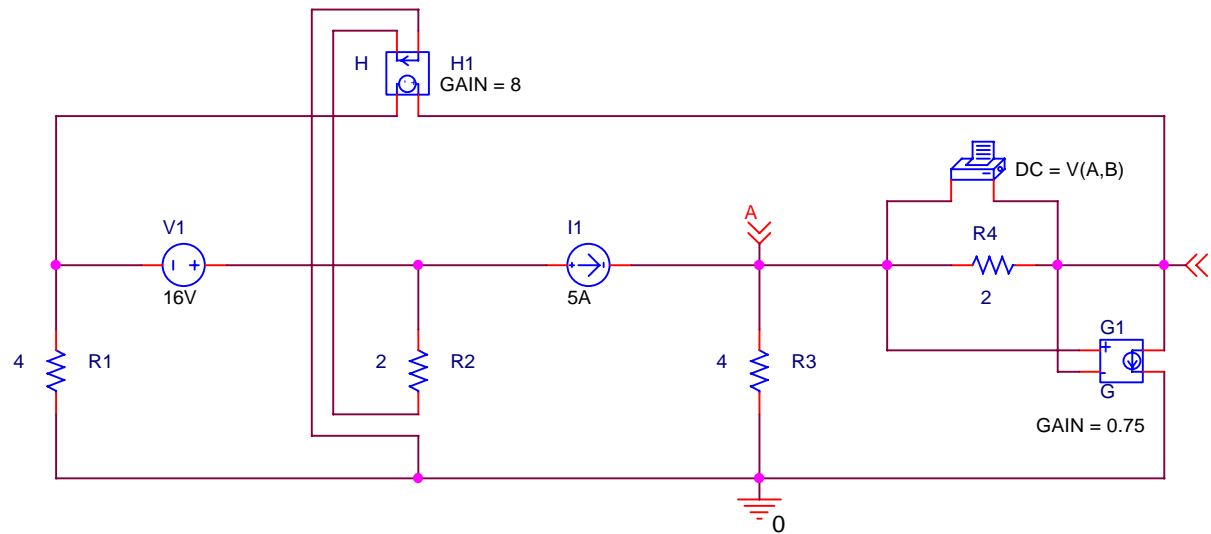


Analyzing Circuits with Dependent Sources

Purpose: Analyze the circuit shown below to determine the voltage $V(A, B)$. Compare the appearance of this circuit to the same problem from a textbook shown on the next page. Dependent sources have a very different appearance.

Analysis: A DC Sweep will be used to vary the independent voltage source from 16V to 16V
(the voltage printer will not work unless a DC sweep is performed).




Notes:

- 1) The 4 types of dependent sources are called E, F, G, and H and are found in the ANALOG library.
 - E = voltage-controlled voltage source
 - F = current-controlled current source
 - G = voltage-controlled current source
 - H = current-controlled voltage source
- 2) When placing dependent sources, keep in mind that the round symbol is the source and the polarity or the arrow are connected to the control variable. Be sure that the correct polarity or current direction are used both for the source and for the control variable.
- 3) Be sure to set the GAIN property on the dependent source to the appropriate value. The default value is 1. The GAIN property is not automatically displayed, so:
 - A) Double-click on the dependent source to edit its properties
 - B) Right-click on the GAIN property in the screen for editing properties and change the Display Format to Name and Value.
 - C) Go back to the schematic and the GAIN property should now be displayed. Double-click on it to change its value.

Title		
<Title>		
Size	Document Number	Rev
A	<Doc>	<RevCode>
Date:	Thursday, February 10	Sheet 1 of 1

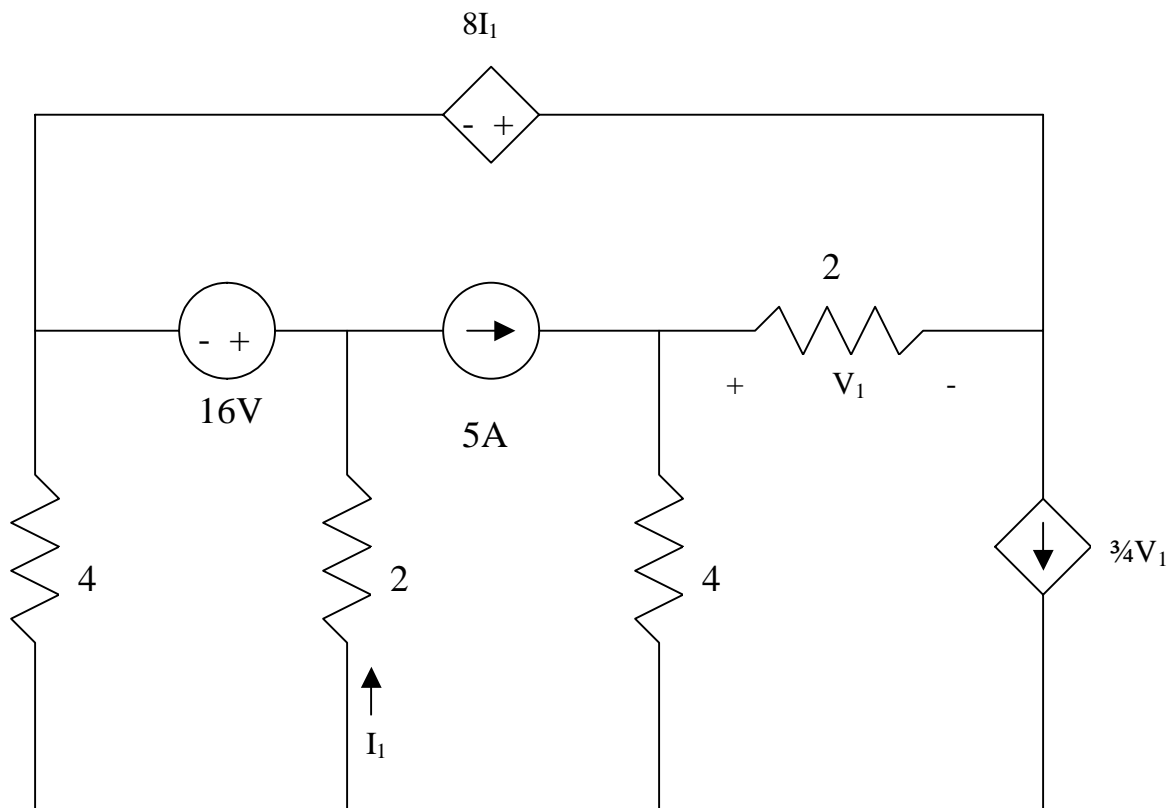Problem 4.33 (from Electric Circuits by Nilsson)
 Find the voltage V_1 .
 (Answer: 8V)



**** 02/10/ 22:16:38 ***** Evaluation PSpice *****

** circuit file for profile: DC Sweep

**** CIRCUIT DESCRIPTION

** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT PROFILES

*Libraries:

* Local Libraries :

* From [PSPICE NETLIST] section of pspiceev.ini file:

.lib nom.lib

*Analysis directives:

.DC LIN V_V1 16V 16V 1

.PROBE

.INC "dependent sources-SCHEMATIC1.net"

**** INCLUDING "dependent sources-SCHEMATIC1.net" ****

* source DEPENDENT SOURCES

R_R1 0 N00081 4
R_R2 N00100 N00037 2
R_R3 0 A 4
R_R4 B A 2
V_V1 N00037 N00081 DC 16V AC 1Vac
I_I1 N00037 A DC 5A AC 1Aac
H_H1 B N00081 VH_H1 8
VH_H1 0 N00100 0V
G_G1 B 0 A B 0.75

.PRINT DC V([A],[B])

.END

**** 02/10/ 22:16:38 ***** Evaluation PSpice *****

** circuit file for profile: DC Sweep

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

V_V1 V(A,B)

1.600E+01 8.000E+00 So V₁ = V(A,B) = 8V

JOB CONCLUDED

TOTAL JOB TIME .26

