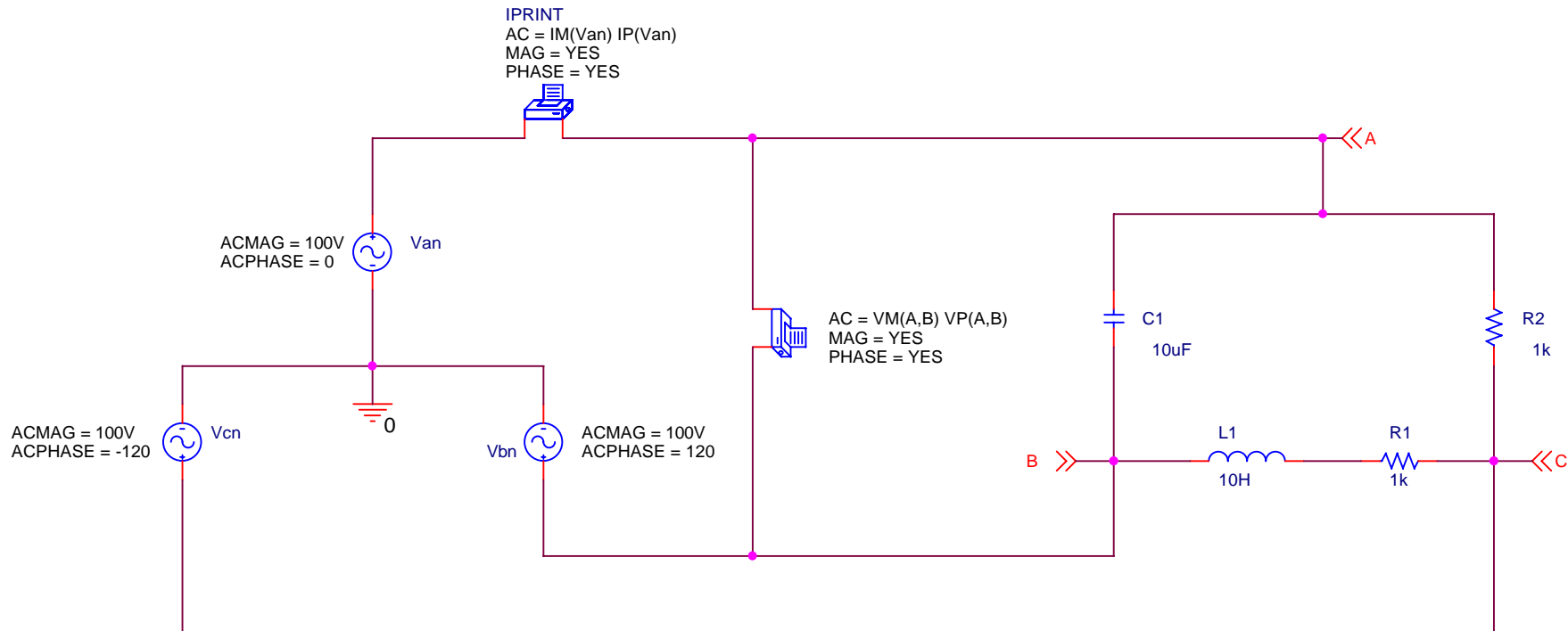


3-Phase Wye-Delta Circuit

Purpose: Determine the line voltage V_{AB} and the line current I_{aA} .

Analysis: Perform an AC SWEEP using a single frequency of 60 Hz.



Note that the generator is balanced, but the load is not balanced. Since the generator is balanced, the magnitude of the line voltage should be $100 \cdot \sqrt{3} = 173.2V$.

Note that OFFPAGE symbols were added so that the nodes could be labeled A, B, and C according to convention.

Edit attributes of parts as follows:

- 1) If the attribute appears next to the part, double click it and then change its value
- 2) If the attribute does not appear next to the part, double click on the part, find the desired attribute, right click on it and select DISPLAY. Then indicate what Display Format is desired. Once the attribute has been displayed, double-click on it and change the value.

Title <Title>		
Size A	Document Number <Doc>	Rev <RevCode>
Date:	Thursday, January 27, 2000	Sheet 1 of 1

**** 01/27/00 23:40:25 ***** Evaluation PSpice (Mar 1999) *****

** circuit file for profile: AC Sweep

**** CIRCUIT DESCRIPTION

** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT PROFILES

*Libraries:

* Local Libraries :

* From [PSPICE NETLIST] section of pspiceev.ini file:
.lib nom.lib

*Analysis directives:

.AC LIN 1 60Hz 60Hz

.PROBE

.INC "wyedelta-SCHEMATIC1.net"

**** INCLUDING wyedelta-SCHEMATIC1.net ****

* source WYEDELTA

V_Van N00058 0 DC 0Vdc AC 100V 0

V_Vcn C 0 DC 0Vdc AC 100V -120

V_Vbn B 0 DC 0Vdc AC 100V 120

C_C1 B A 10uF

L_L1 B N00087 10H

R_R1 N00087 C 1k

R_R2 C A 1k

.PRINT AC

+ VM([A],[B])

+ VP([A],[B])

V_PRINT2 N00058 A 0V

.PRINT AC

+ IM(V_PRINT2)

+ IP(V_PRINT2)

**** RESUMING "wyedelta-SCHEMATIC1-AC Sweep.sim.cir" ****

.INC "wyedelta-SCHEMATIC1.als"

**** RESUMING "wyedelta-SCHEMATIC1-AC Sweep.sim.cir" ****

.END

**** 01/27/00 23:40:25 ***** Evaluation PSpice (Mar 1999) *****

** circuit file for profile: AC Sweep

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(A)	0.0000	(B)	0.0000	(C)	0.0000	(N00058)	0.0000
(N00087)	0.0000						

VOLTAGE SOURCE CURRENTS	
NAME	CURRENT
V_Van	0.000E+00
V_Vcn	0.000E+00
V_Vbn	0.000E+00
V_PRINT2	0.000E+00

TOTAL POWER DISSIPATION 0.00E+00 WATTS

**** 01/27/00 23:40:25 ***** Evaluation PSpice (Mar 1999) *****

** circuit file for profile: AC Sweep

**** AC ANALYSIS TEMPERATURE = 27.000 DEG C

FREQ	VM(A,B)	VP(A,B)	
6.000E+01	1.732E+02	-3.000E+01	So $V_{AB} = 173.2 / -30^\circ V$

**** 01/27/00 23:40:25 ***** Evaluation PSpice (Mar 1999) *****

** circuit file for profile: AC Sweep

**** AC ANALYSIS TEMPERATURE = 27.000 DEG C

FREQ	IM(V_PRINT2)	IP(V_PRINT2)	
6.000E+01	8.076E-01	5.384E+01	So $I_{aA} = 0.8076 / 53.84^\circ A$

JOB CONCLUDED

TOTAL JOB TIME .04

