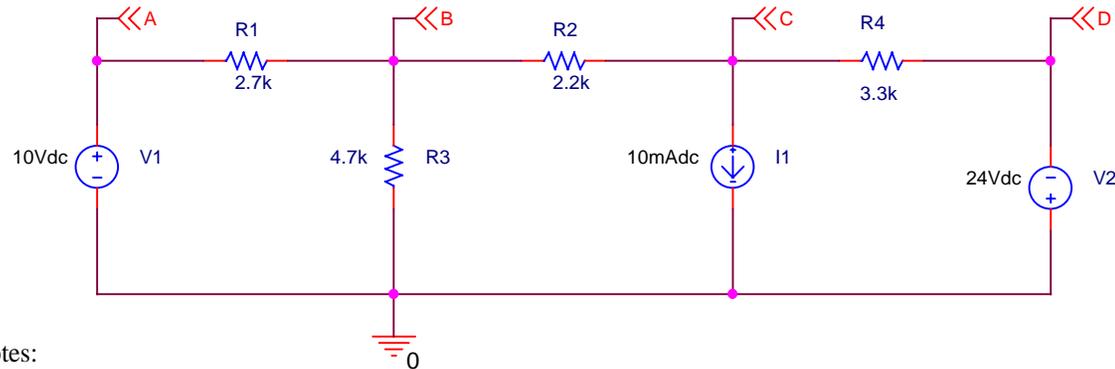


DC Circuit - Determining Node Voltages

Purpose: Determine the node voltages in the circuit shown below.

Analysis: The simplest type of analysis in PSPICE is a bias point analysis. This type of analysis determines node voltages. Currents through voltage sources and total circuit power dissipation are also automatically determined.



Notes:

- 1) All circuits must include a ground symbol. Use the GND symbol from the toolbar (pick that ground symbol labeled 0).
- 2) The voltages sources are part VSRC from the SOURCE library.
- 3) Parts may be rotated using Ctrl + R. Alternately, right-click on the part and pick ROTATE or MIRROR.
- 4) Note that the current source has the units mA dc. PSPICE ignores all letters after the first letter m, which is a valid SI prefix. So the current could have just as easily have been labeled 10milliamperes. Be sure not to include any spaces.
- 5) PSPICE uses its own node numbering technique and it is often not apparent what node numbers will be used. Specific node names can be assigned using OFFPAGE symbols (>>C on the toolbar). Note that nodes A - D have been labeled above and will be referred to in the OUT file.

3 Basic Steps in analyzing a circuit using ORCAD Capture.


- 1) Draw the schematic
 - A) Start ORCAD Capture. Pick FILE - NEW - PROJECT from the main menu.
 - B) Enter a project name. Pick Analog or Mixed-Signal Circuit Wizard under "Create a new project using." See attached page as an example.
 - C) Add any necessary libraries. The default libraries are often sufficient, but the EVAL library is sometimes needed for digital parts, switches, op amps, and more.
 - D) A blank schematic screen will appear. Draw the schematic.
- 2) Create the Simulation Profile.
 - A) Pick PSPICE - NEW SIMULATION PROFILE from the main menu.
 - B) Choose a name for the Simulation Profile. For example, the name BIAS was used for a bias point analysis (see attached page).
 - C) Select the type of analysis (see attached page as an example).
- 3) Analyze the circuit.
 - A) Pick PSPICE - RUN from the main menu.
 - B) Once the analysis screen appears and the analysis is completed, select VIEW - OUTPUT FILE to see the results. See the attached OUTPUT FILE.

Title		
<Title>		
Size	Document Number	Rev
A	<Doc>	<RevCode>
Date:	Saturday, February 05	Sheet 1 of 1


3 Basic Steps in analyzing a circuit using ORCAD Capture.

1) Draw the schematic

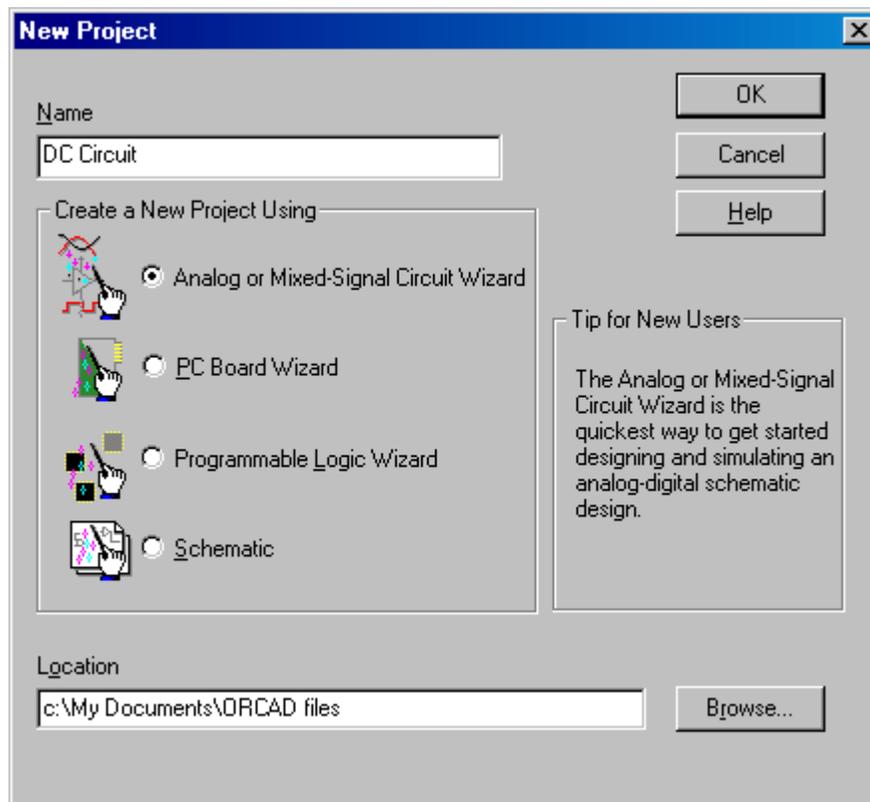- A) Start ORCAD Capture. Pick FILE – NEW – PROJECT from the main menu.
- B) Enter a project name. Pick Analog or Mixed-Signal Circuit Wizard under Create a New Project Using.




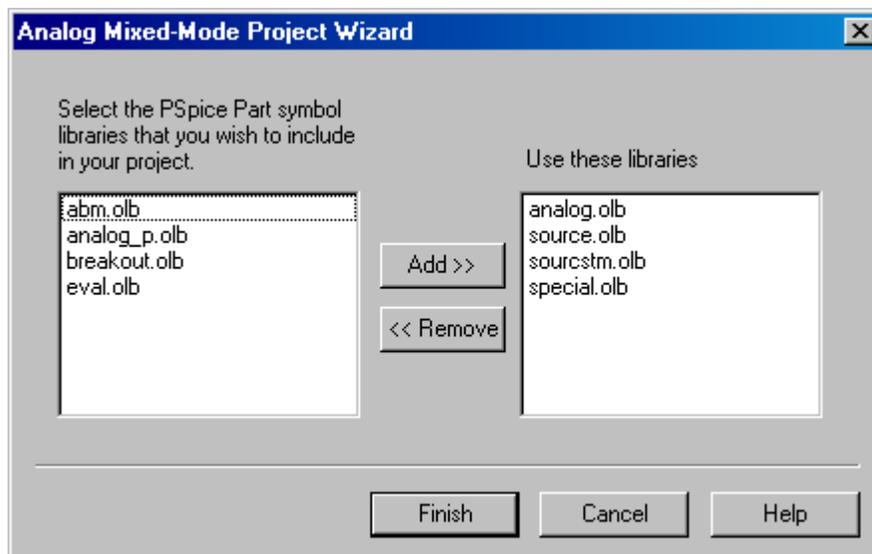- C) Add any necessary libraries. The default libraries are often sufficient, but the EVAL library is sometimes needed for digital parts, switches, op amps, and more.




- D) A blank schematic page will appear. Draw the schematic.

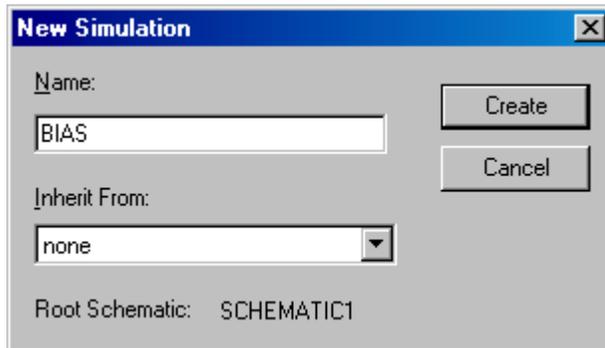- 2) Create the simulation Profile.
 - A) Pick PSPICE – NEW SIMULATION PROFILE from the main menu.
 - B) Choose a name for the Simulation Profile. The name BIAS was chosen below since a Bias-point analysis will be performed.



- C) Select the type of analysis.

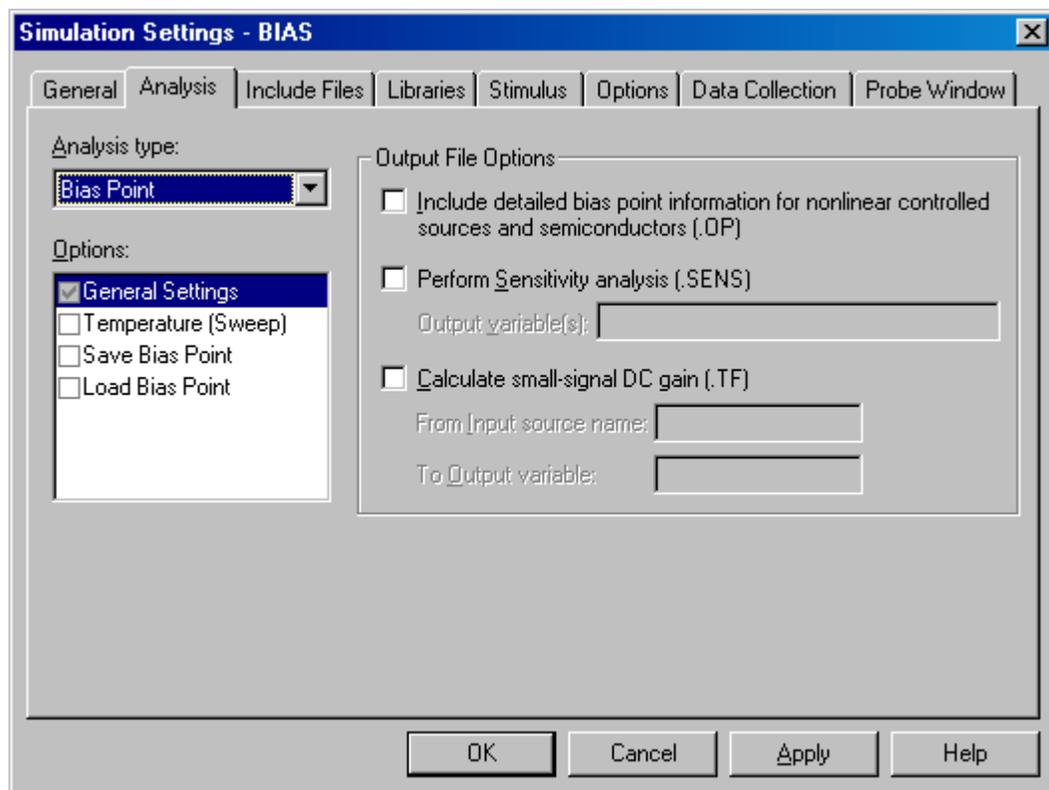

- 3) Analyze the circuit.
 - A) Pick PSPICE – RUN from the main menu.
 - B) Once the analysis screen appears and the analysis is complete, view the OUTPUT file to see the results. See the attached OUTPUT file.

**** 02/05/ 22:50:44 ***** Evaluation PSpice *****

** circuit file for profile: BIAS

**** CIRCUIT DESCRIPTION

** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT PROFILES

*Libraries:

* Local Libraries :

* From [PSPICE NETLIST] section of pspiceev.ini file:

.lib nom.lib

*Analysis directives:

.PROBE

.INC "dc circuit-SCHEMATIC1.net"

**** INCLUDING "dc circuit-SCHEMATIC1.net" ****

* source DC CIRCUIT

V_V2 0 D DC 24Vdc AC 1Vac

V_V1 A 0 DC 10Vdc AC 1Vac

R_R1 A B 2.7k

R_R2 B C 2.2k

R_R3 0 B 4.7k

R_R4 C D 3.3k

I_I1 C 0 DC 10mAdc AC 1Aac

.END

**** 02/05/ 22:50:44 ***** Evaluation PSpice *****

** circuit file for profile: BIAS

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE

(A) 10.0000 (B) -8.7063 (C) -28.0240 (D) -24.0000

Note: Node voltages are shown using the letters assigned using OFFSET symbols

VOLTAGE SOURCE CURRENTS

NAME CURRENT

V_V2 1.219E-03

V_V1 -6.928E-03

Note: The current through voltage sources is shown

TOTAL POWER DISSIPATION 4.00E-02 WATTS

Note: Total power dissipation is shown

JOB CONCLUDED

TOTAL JOB TIME .27