File: Hazards1

## **PSPICE Example: Correcting a Static-1 Hazard**

A minimal Sum of Products (SOP) expression of the function  $F(A,B,C) = \Sigma(3,4,6,7)$  can be found using a Karnaugh map as follows:

ABC	00	01	11	10
0			1	
1	1		1	1


The resulting expression is: F(A,B,C) = AB' + BC (minimal SOP)

One problem with the implementation above is that the circuit has a static-1 hazard. In particular, the output should remain logic 1 as the input changes from input minterm 7 to minterm 6, but it actually goes briefly low. This problem can be corrected by adding a "consensus term". Minterm 6 is covered by the product term AC' and minterm 7 is covered by the product term BC. The term AC' has additional propagation delay since C is inverted, resulting in a "glitch" in the output. The consensus term AB overlaps the other two product terms and eliminates the glitch. The new Karnaugh map is shown below:

ABC	00	01	11	10
0			1	
1	1		1	

The resulting expression is: F(A,B,C) = AB' + BC + AB (static-1 hazard eliminated)

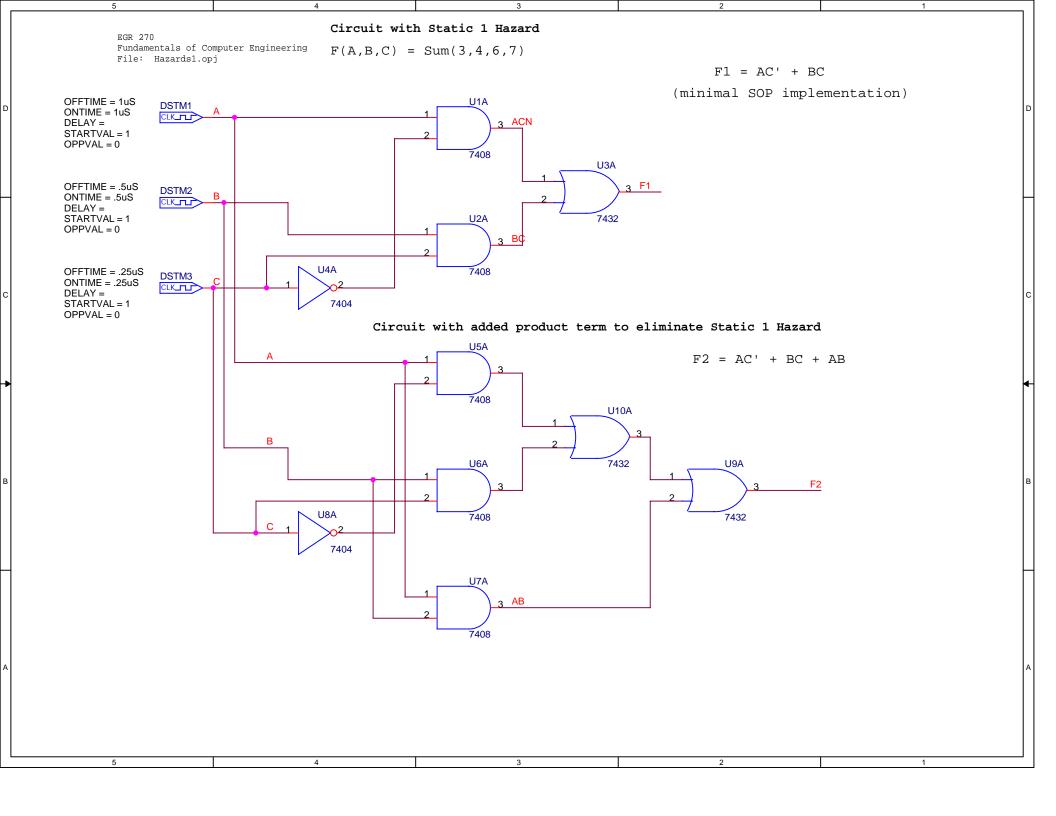The example above is implemented on the following pages using PSPICE where a timing diagram is used to reveal the glitch in the original circuit and to show that the glitch has been removed in the modified circuit.



Temperature: 27.0

