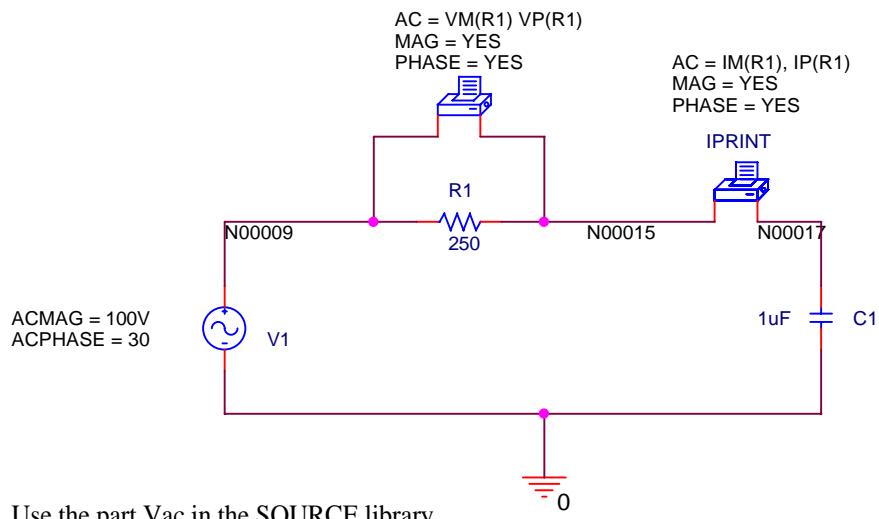


AC Circuit Analysis using Phasors

Purpose: To analyze the circuit below using a frequency of 1 kHz and to determine the magnitude and phase angle of the current and the resistor voltage.

Analysis type: AC Sweep



Use the part Vac in the SOURCE library
 Phase angle is in degrees. Default value is zero degrees.

To display a node value, double-click on the wire, then right-click on the Name, and choose Display and pick Value Only as the Display Format.

Edit attributes of parts as follows:



- 1) If the attribute appears next to the part, double click it and then change its value
- 2) If the attribute does not appear next to the part, double click on the part, find the desired attribute, right click on it and select DISPLAY. Then indicate what Display Format is desired. Once the attribute has been displayed, double-click on it and change the value.

Use the part VPRINT2 in the SPECIAL library for the voltage printer.

Use the part IPRINT in the SPECIAL library for the current printer.

Note: Use the following notation with printers:
 VM = voltage magnitude
 VP = voltage phase
 IM = current magnitude
 IP = current phase

Title		<Title>
Size A	Document Number <Doc>	Rev <RevCode>
Date: Tuesday, January 25, 2000	Sheet 1 of 1	

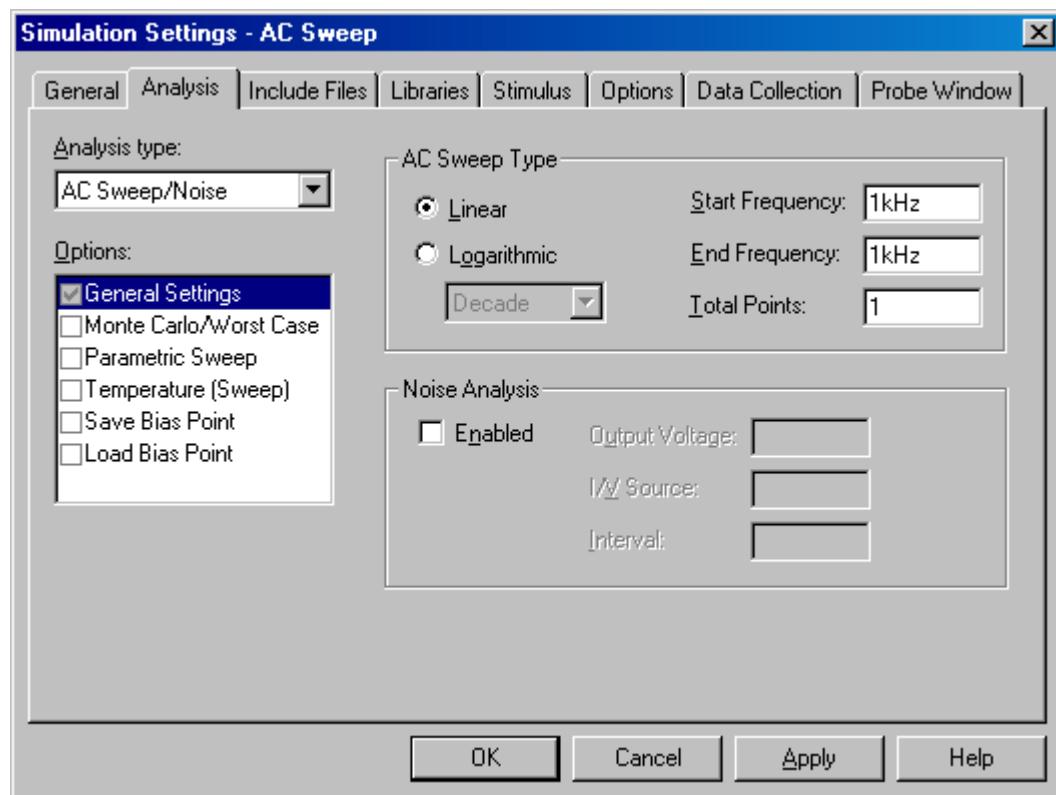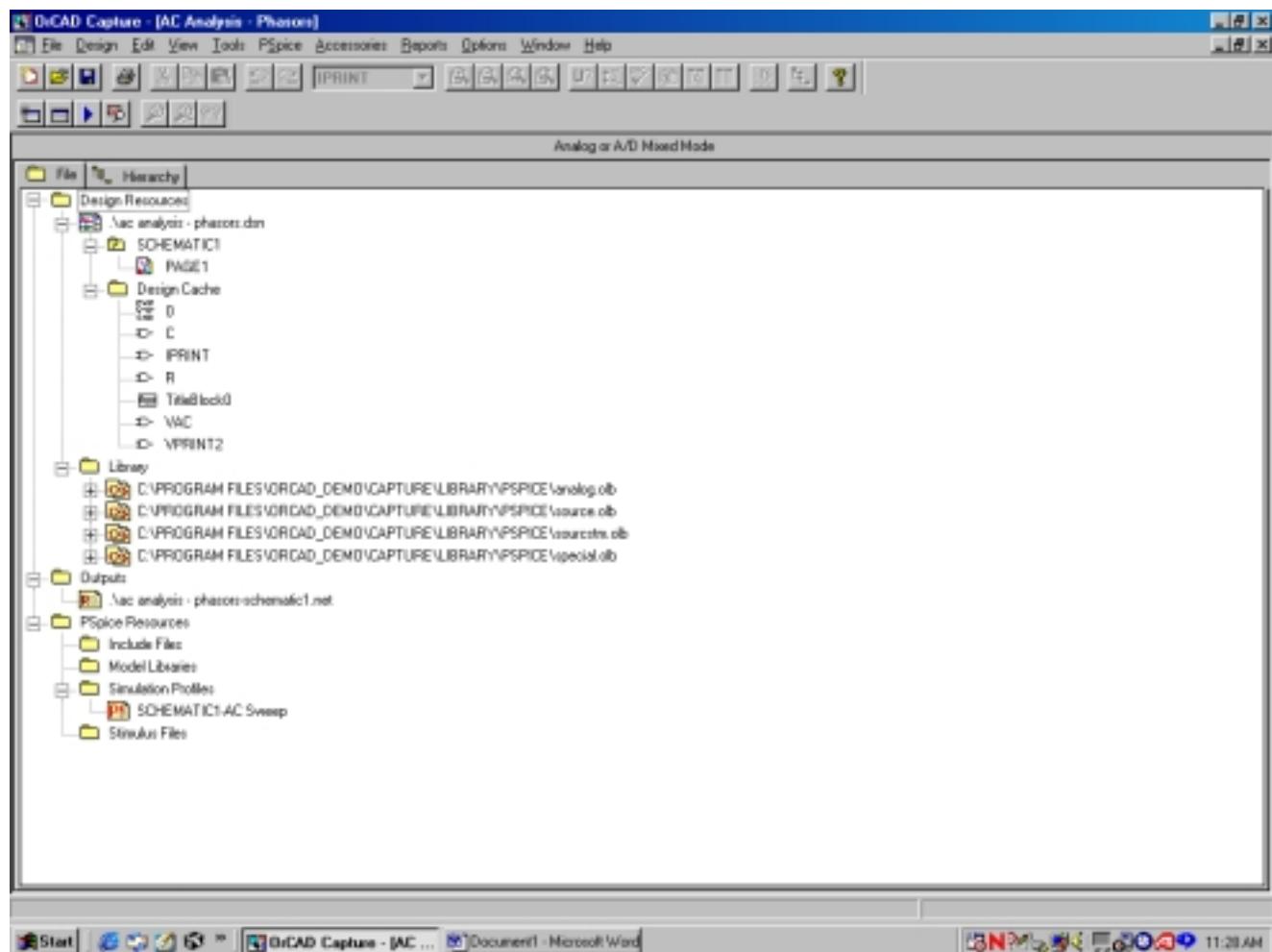

```

***** 01/25/00 11:25:16 ***** Evaluation PSpice (Mar 1999) *****

** circuit file for profile: AC Sweep

**** CIRCUIT DESCRIPTION
*****
** WARNING: THIS AUTOMATICALLY GENERATED FILE MAY BE OVERWRITTEN BY SUBSEQUENT
PROFILES

*Libraries:
* Local Libraries :
* From [PSPICE NETLIST] section of pspiceev.ini file:
.lib nom.lib

*Analysis directives:
.AC LIN 1 1kHz 1kHz
.PROBE
.INC "ac analysis - phasors-SCHEMATIC1.net"

**** INCLUDING "ac analysis - phasors-SCHEMATIC1.net" ****
* source AC ANALYSIS - PHASORS
V_V1      N00009 0 DC 0Vdc AC 100V 30
R_R1      N00009 N00015 250
C_C1      N00017 0 1uF

.PRINT      AC
+ VM([N00009],[N00015])
+ VP([N00009],[N00015])
V_PRINT2   N00015 N00017 0V

.PRINT      AC
+ IM(V_PRINT2)
+ IP(V_PRINT2)

**** RESUMING "ac analysis - phasors-SCHEMATIC1-AC Sweep.sim.cir" ****
.INC "ac analysis - phasors-SCHEMATIC1.als"

**** INCLUDING "ac analysis - phasors-SCHEMATIC1.als" ****
.ALIASES
V_V1      V1(+=N00009 -=0 )
R_R1      R1(1=N00009 2=N00015 )
C_C1      C1(1=N00017 2=0 )
V_PRINT2  PRINT2(1=N00015 2=N00017 )

.ENDALIASES

**** RESUMING "ac analysis - phasors-SCHEMATIC1-AC Sweep.sim.cir" ****
.END

***** 01/25/00 11:25:16 ***** Evaluation PSpice (Mar 1999) *****

** circuit file for profile: AC Sweep

```

```

****      SMALL SIGNAL BIAS SOLUTION      TEMPERATURE = 27.000 DEG C
*****
NODE    VOLTAGE     NODE    VOLTAGE     NODE    VOLTAGE     NODE    VOLTAGE
(N00009)   0.0000 (N00015)   0.0000 (N00017)   0.0000

VOLTAGE SOURCE CURRENTS
NAME          CURRENT

V_V1          0.000E+00
V_PRINT2      0.000E+00

TOTAL POWER DISSIPATION  0.00E+00 WATTS

**** 01/25/00 11:25:16 **** Evaluation PSpice (Mar 1999) ****
** circuit file for profile: AC Sweep

****      AC ANALYSIS      TEMPERATURE = 27.000 DEG C
*****
FREQ        VM(N00009,N00015)VP(N00009,N00015)

1.000E+03   8.436E+01   6.248E+01      So V = 84.36/62.48° A

**** 01/25/00 11:25:16 **** Evaluation PSpice (Mar 1999) ****
** circuit file for profile: AC Sweep

****      AC ANALYSIS      TEMPERATURE = 27.000 DEG C
*****
FREQ        IM(V_PRINT2)IP(V_PRINT2)

1.000E+03   3.374E-01   6.248E+01      So I = 0.3374/62.48° A

JOB CONCLUDED

TOTAL JOB TIME      .03

```